

Lecture 15: Buffering

Matthew Guthaus

Professor

UCSC, Computer Science & Engineering

<http://vlsida.soe.ucsc.edu>

mrg@ucsc.edu



Today's Lecture

- Cascaded Buffers
 - Driving large capacitive loads
- Repeaters
 - Driving long wires
- Generalized Buffering
 - Capacitive shielding
 - Driving fanout with varying criticalities
 - Van Ginneken algorithm




Today's Lecture

- Cascaded Buffers
 - Driving large capacitive loads
- Repeaters
 - Driving long wires
- Generalized Buffering
 - Capacitive shielding
 - Driving fanout with varying criticalities
 - Van Ginneken algorithm




Linear Gate Delay Model

 

$$d \propto \frac{R}{s} (sC_p + C_{out})$$




- Sutherland, Ivan E.; Sproull, Robert F.; Harris, David F. (1999). *Logical Effort: Designing Fast CMOS Circuits*. Morgan Kaufmann. ISBN 1-55860-557-6.

Self Loading: Another View

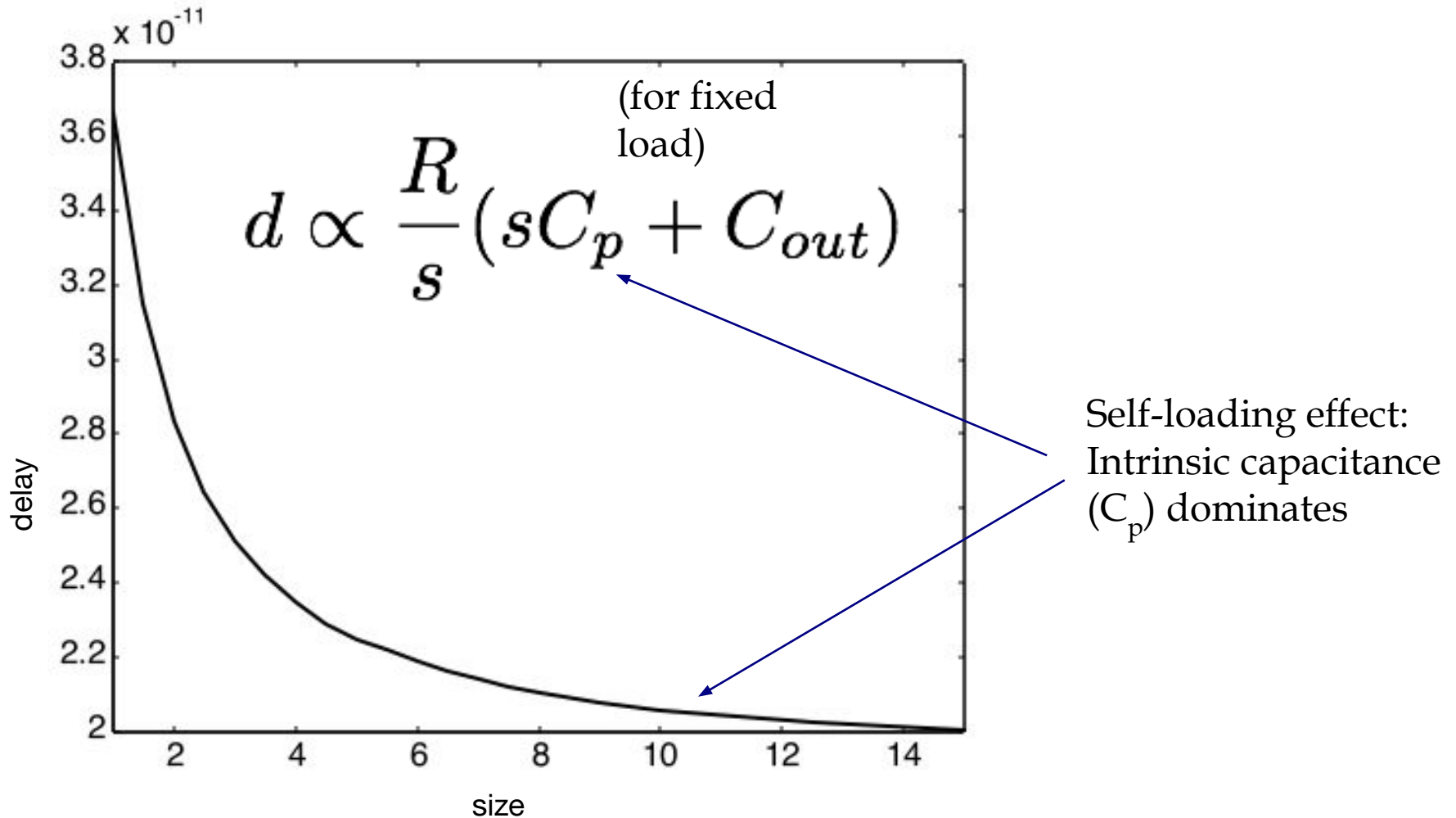


Intuition Check

   - Driving a big capacitor requires a big buffer/inverter
- A big buffer/inverter has a big input capacitance and will slow the previous stage
- What to do?



Multistage drivers

 - Each stage “ramps up” to a bigger buffer (or inverter)
 - Small capacitance on first stage
 - Big buffer on last stage
- What is the ideal “ramp up”?



Best Ratio of Sizes

- Formulate equation with N stages with linear delay model and solve to minimize delay

- Has no closed-form solution


$$P_{inv} + \rho (1 - \ln \rho) = 0$$

- P_{inv} is the parasitic delay (RC_p)
- Neglecting parasitic delay ($P_{inv} = 0$)
 - $\rho = 2.718$ (e)
- For $P_{inv} = 1$, solve numerically
 - $\rho = 3.59$

- Sutherland, Ivan E.; Sproull, Robert F.; Harris, David F. (1999). *Logical Effort: Designing Fast CMOS Circuits*. Morgan Kaufmann. ISBN 1-55860-557-6.

Best Number of Stages


 
- How many stages should a driver use?
 - Minimizing number of stages is not always fastest
 - Each stage should “ramp up” equally
- Example: drive 64-bit datapath with unit inverter
- Brute force:
 - N is number of stages
 - f is ratio of output to input “size”
 - D is delay



Best Number of Stages

- Equally divide the ratio of sizes
 - $\log_{3.59}(64) \approx \log_4(64) = 3$
- How to compute arbitrary logs:
 - $\log_4(64) = \log(64)/\log(4)$

$$\frac{\partial D}{\partial N} = 0$$

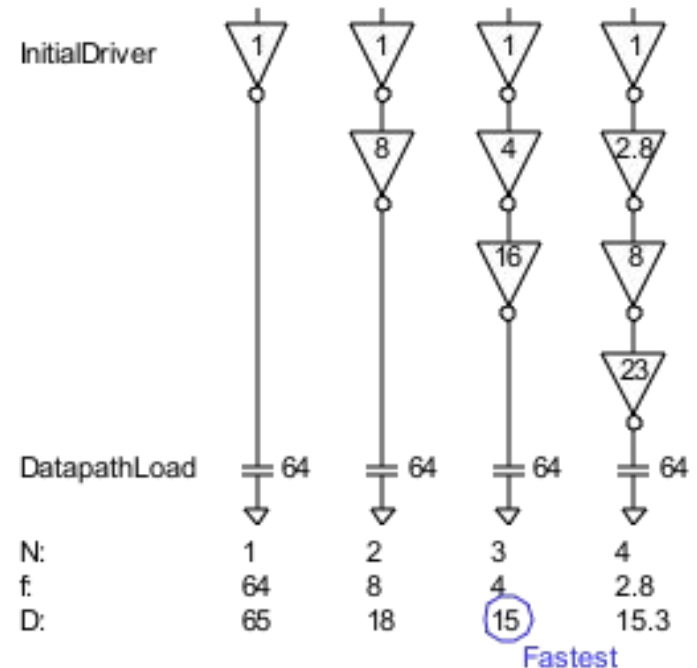 


- Sutherland, Ivan E.; Sproull, Robert F.; Harris, David F. (1999). *Logical Effort: Designing Fast CMOS Circuits*. Morgan Kaufmann. ISBN 1-55860-557-6.

Today's Lecture

- Cascaded Buffers
 - Driving large capacitive loads
- Repeaters
 - Driving long wires
- Generalized Buffering
 - Capacitive shielding
 - Driving fanout with varying criticalities
 - Van Ginneken algorithm



Why is this trend?

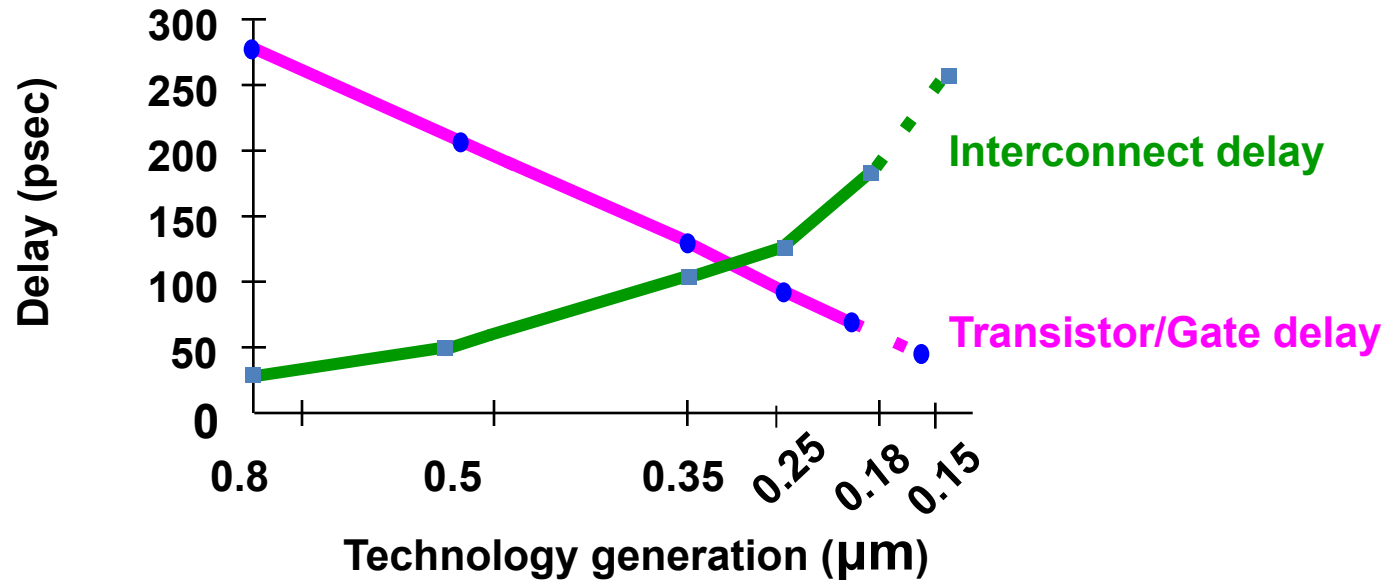

Source: Gordon Moore, Chairman Emeritus, Intel Corp.




Dennard Scaling


- **Ideal process scaling:**

- Device geometries shrink by s ($= 0.7x$)
 - “Moore’s Law”
 - Device delay shrinks by s
- Wire geometries shrink by s (or σ)
 - **Unit resistance R : $\rho/(ws.hs) = r/s^2$**
 - **Unit coupling capacitance C_c : $(hs)/(Ss)$**
 - **Resistance doubled, capacitance roughly unchanged for unit length**
 - How about the change in wire length?

$$s^2 = 0.7^2 = 0.49$$

 

Wire length scaling

 

- Global (long) interconnect lengths don't shrink
 - Global interconnect link cells far apart
 - Maximum chip size stays roughly the same (more transistors though!)
- Local (short) interconnect lengths shrink by s
 - Local interconnects link cells nearby



Interconnect delay scaling


- **Delay of a wire of length l :**
 $\tau_{int} = (rl)(cl) = rcl^2$ (a quadratic function of length)
- **Local interconnects :**
 $\tau_{int} : (r/s^2)(c)(ls)^2 = rcl^2$
 - **Local interconnect delay unchanged (s^2 cancels out)**
- **Global interconnects :**
 $\tau_{int} : (r/s^2)(c)(l)^2 = (rcl^2)/s^2$
 - **Global interconnect delay doubled – unsustainable!**
- ***Interconnect delay increasingly more dominant***



Elmore Delay for Wire


unit wire capacitance c

unit wire resistance r

 


$$delay = \frac{(xr)(xc)}{2} + (xr)C$$

Above assumes a "pi" model for the wire

 

Elmore Delay for Buffer

 

$$\text{delay}(u, v) = R(b)C$$

$$C(u) = C(b)$$


Input capacitance

Driving resistance




Elmore Delay for A Circuit

 - Delay = $\sum_{\text{all } R_i} \sum_{\text{all } C_j \text{ downstream from } R_i} R_i * C_j$
- Elmore delay to n1 $R(B) * (C1 + C2)$
- Elmore delay to n2 $R(B) * (C1 + C2) + R(w) * C2$




Unbuffered Wire Delay

 

$$t_{unbuf} = R(cx + C) + rx(cx/2 + C)$$




Buffered Wire Delay

 


$$t_{buf} = 2R(cx/2 + C) + rx(cx/4 + C)$$



Buffered global interconnects: Intuition

 
 
$$\text{Interconnect delay} = r.c.l^2/2$$



$$\text{Interconnect delay} = \sum r.c.l_j^2/2 < r.c.l^2/2 \quad (\text{where } l = \sum l_j)$$

since $\sum (l_j^2) < (\sum l_j)^2$

(Of course, we need to consider buffer delay as well)



Buffers Reduce Wire Delay


$$t_{unbuf} = R(cx + C) + rx(cx/2 + C)$$

$$t_{buf} = 2R(cx/2 + C) + rx(cx/4 + C)$$

$$t_{buf} - t_{unbuf} = RC - rcx^2/4$$

Buffer delay

Reduced wire delay

 

When does it make sense to use a buffer? $x = ?$



What is the optimal length?

- Can compute based on R, C of wire and gate
- However, it is ok to approximate and loss of delay is not bad
 - ~0.5mm?
 - A few 100um?
- In general, the tools approach it in another way.



Buffer Placement

- The previous formulations assume that you can put a buffer anywhere.
 - What if there are a limited number of open spaces?
- New problem: Timing driven buffer placement and sizing.
 - Uses Static Timing Analysis!




Today's Lecture


- Cascaded Buffers
 - Driving large capacitive loads
- Repeaters
 - Driving long wires
- Generalized Buffering
 - Capacitive shielding
 - Driving fanout with varying criticalities
 - Van Ginneken algorithm




RAT: Required Arrival Time

 

Wire delay = 80

 


Slack: RAT - AT

 



Minimizing circuit delay = maximizing RAT at driver = maximizing slack at driver



An Example for Buffer Insertion

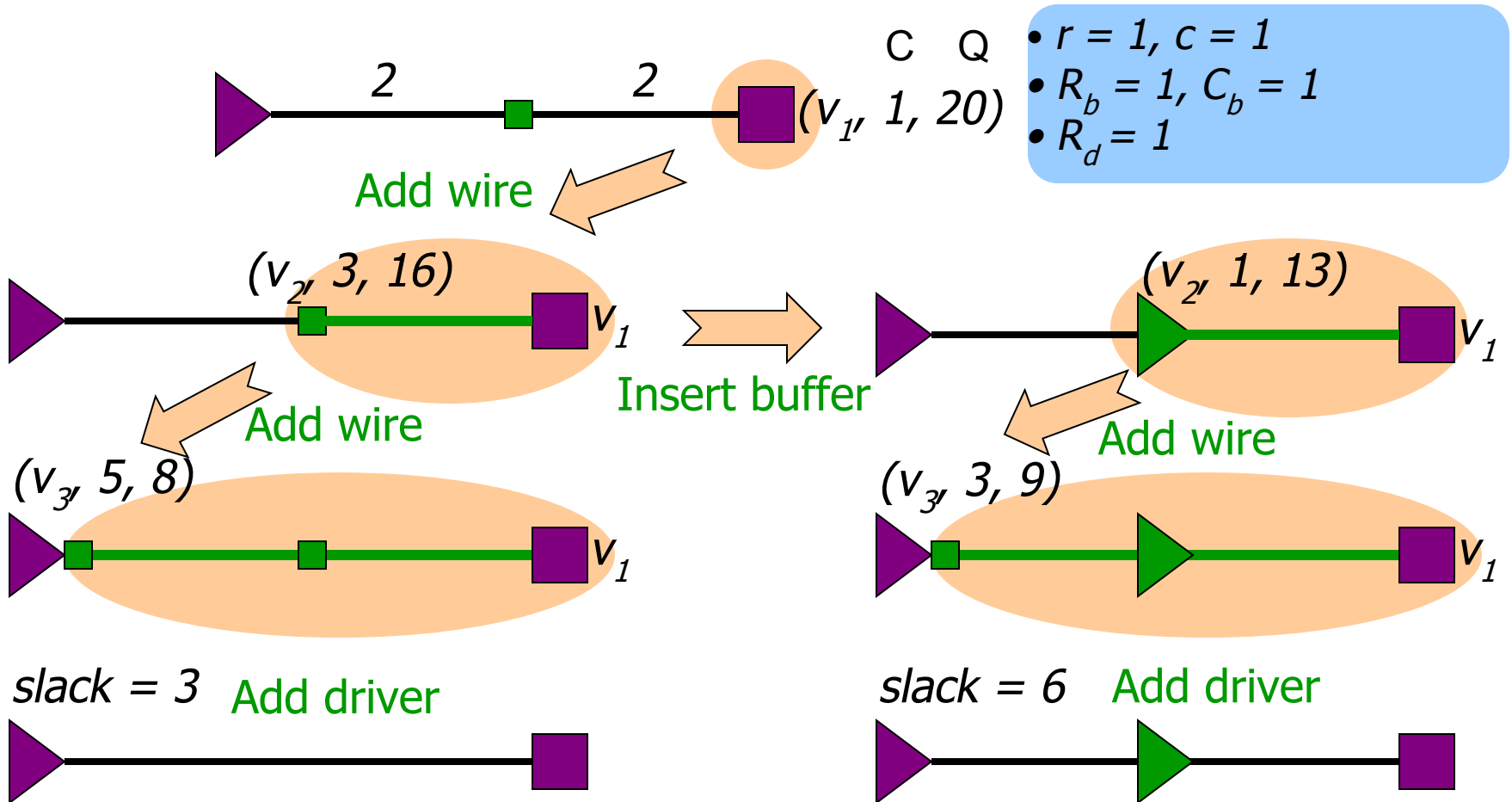


Capacitance Shielding

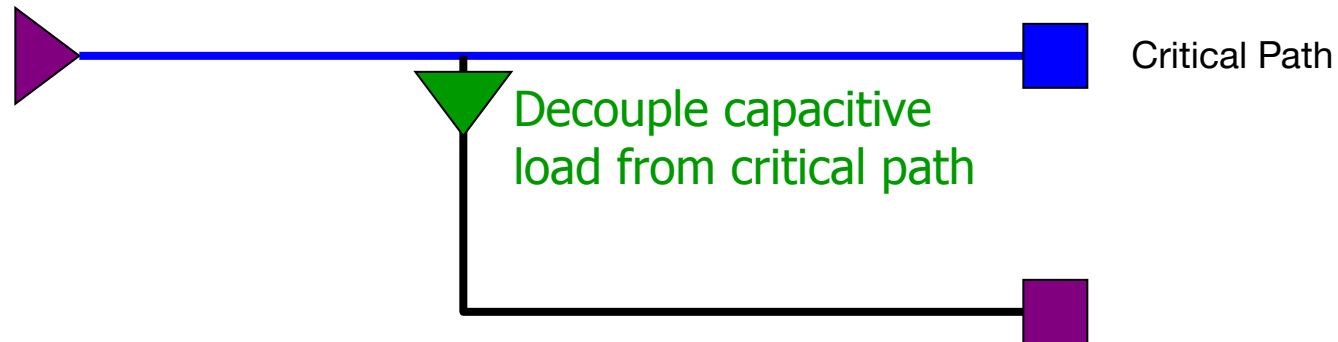 

Makes sense if buffer input capacitance is less than fanout cap and wire



Motivation for Problem Formulation

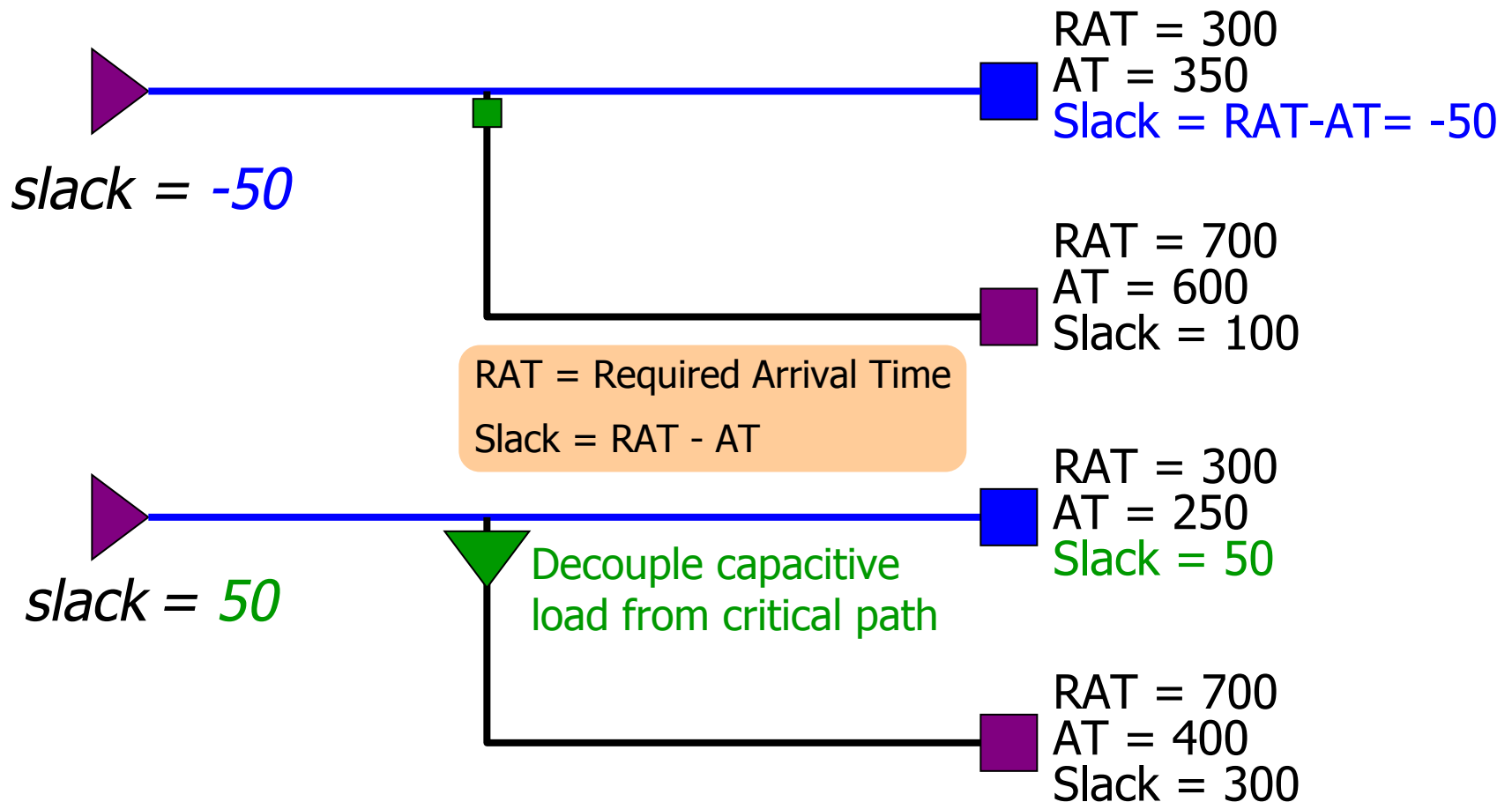


We need to maximum slack or RAT at driver




General Timing Driven Buffering Problem

 - Given
 - A Steiner tree
 - RAT at each sink
 - A buffer type
 - RC parameters
 - Candidate buffer locations
- Find buffer insertion solution such that the slack (or RAT) at the driver is maximized




Candidate Buffering Solution

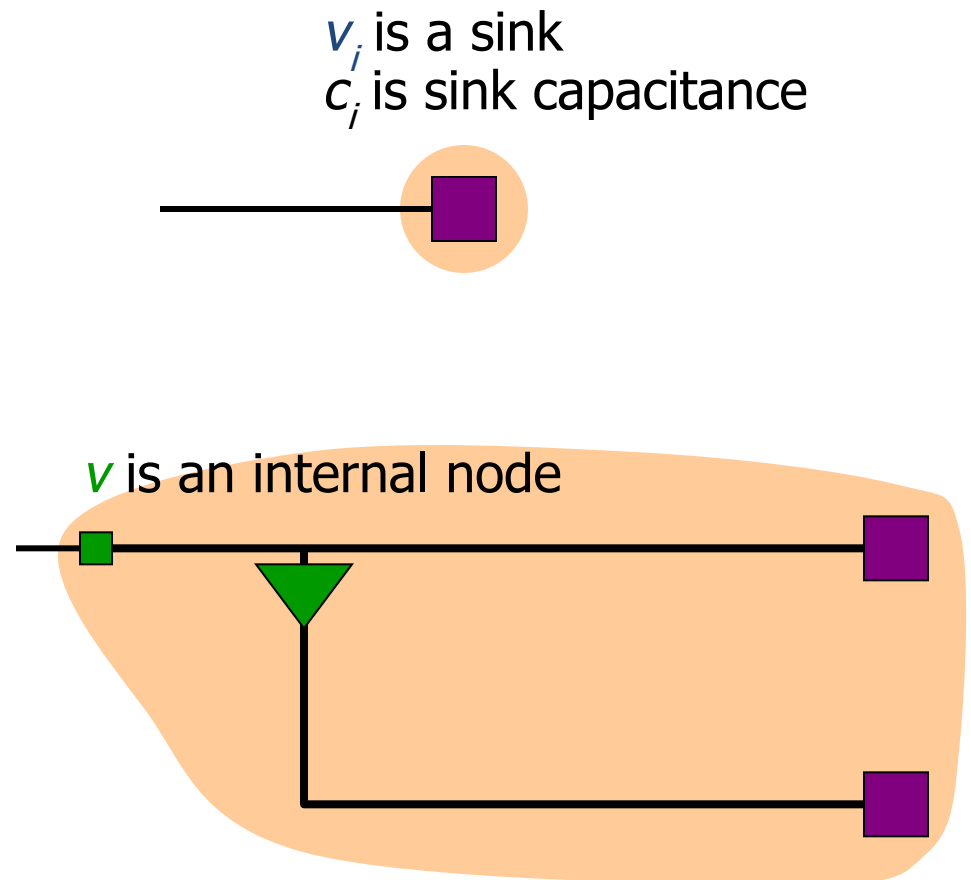- Definition
- Each candidate solution is associated with
 - v_i : a node
 - c_i : downstream capacitance
 - q_i : RAT




Van Ginneken's Algorithm

 


Candidate solutions are propagated toward the source



Generating Candidates

 

Exponential Runtime

 

n candidate buffer locations lead to 2^n solutions




Solution Pruning

- Two candidate solutions
 - (v, c_1, q_1)
 - (v, c_2, q_2)
- Solution 1 is inferior if
 - $c_1 \geq c_2$: larger load
 - and $q_1 \leq q_2$: tighter timing
- **I.e., it keeps “pareto optimal” solutions only!**




Pruning When Insert Buffer

 

They have the same load cap C_b
only the one with max q is kept




Pruning Candidates

 


Both (a) and (b) “look” the same to the source.

Throw out the one with the worse slack

 


Candidate Example Continued

 

Candidate Example Continued

After pruning

 

At driver, compute which candidate maximizes slack. Result is optimal.



Next Lecture

- Chip finishing

